

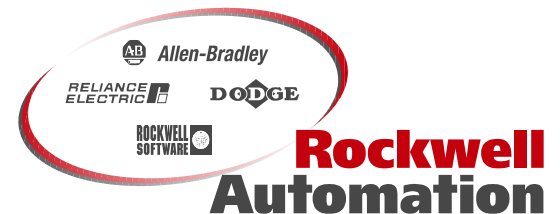
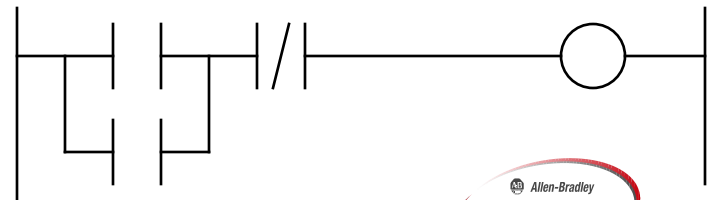
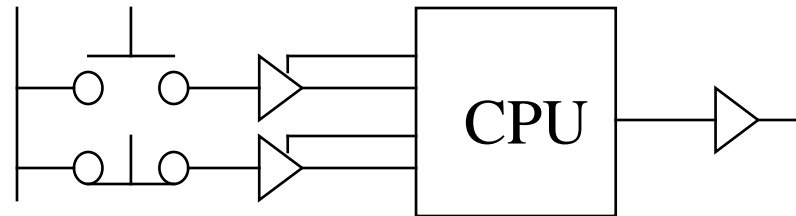


Introduction to IEC1131-3 Ladder Diagram

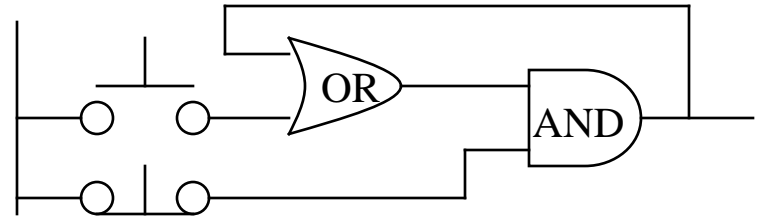


Origins of Ladder Diagram

- The Ladder Diagram (LD) programming language originated from the graphical representation used to design an electrical control system
 - Control decisions were made using relays
- After a while Relays were replaced by logic circuits
 - Logic gates used to make control decisions
- Finally CPUs were added to take over the function of the logic circuits
 - I/O Devices wired to buffer transistors
 - Control decisions accomplished through programming
- Relay Logic representation (or LD) was developed to make program creation and maintenance easier
 - Computer based graphical representation of wiring diagrams that was easy to understand
 - Reduced training and support cost

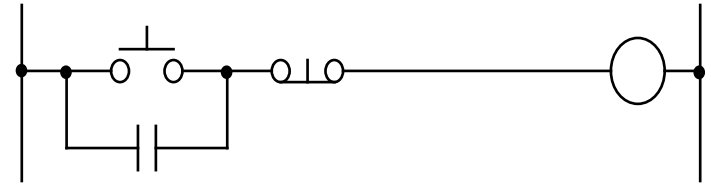


What is a Rung?

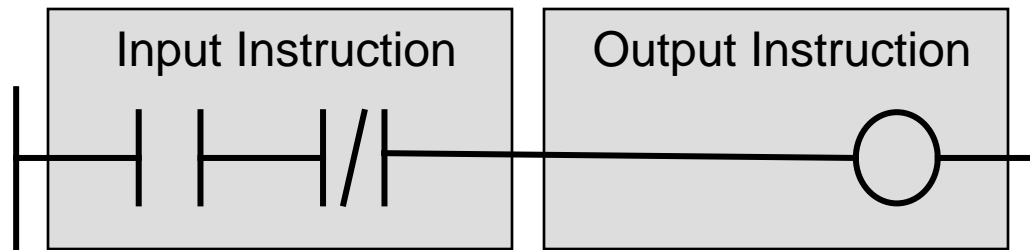- A rung of ladder diagram code can contain both input and output instructions
 - Input instructions perform a comparison or test and set the rung state based on the outcome
 - Normally left justified on the rung
 - Output instructions examine the rung state and execute some operation or function
 - In some cases output instructions can set the rung state
 - Normally right justified on the rung



Series Vs Parallel Operations

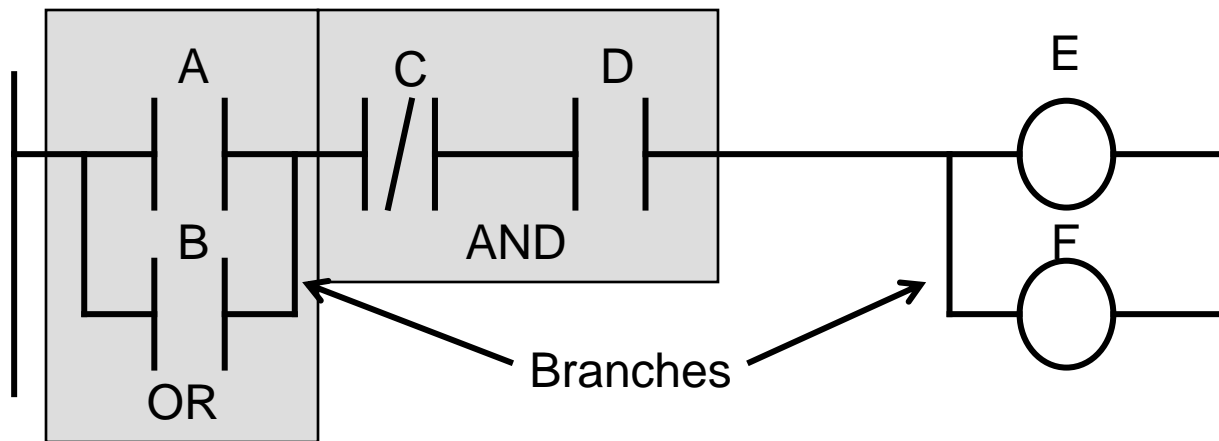
- Ladder Diagram input instructions perform logical AND and OR operations in an easy to understand format
 - If all Input Instructions in series must all be true for outputs to execute (AND)
 - If any input instruction in parallel is true, the outputs will execute (OR)
- Paralleling outputs allows multiple operations to occur based on the same input criteria



IF ((A OR B) AND (NOT C) AND D) THEN E=1; F=1 END_IF

Ladder Logic Execution

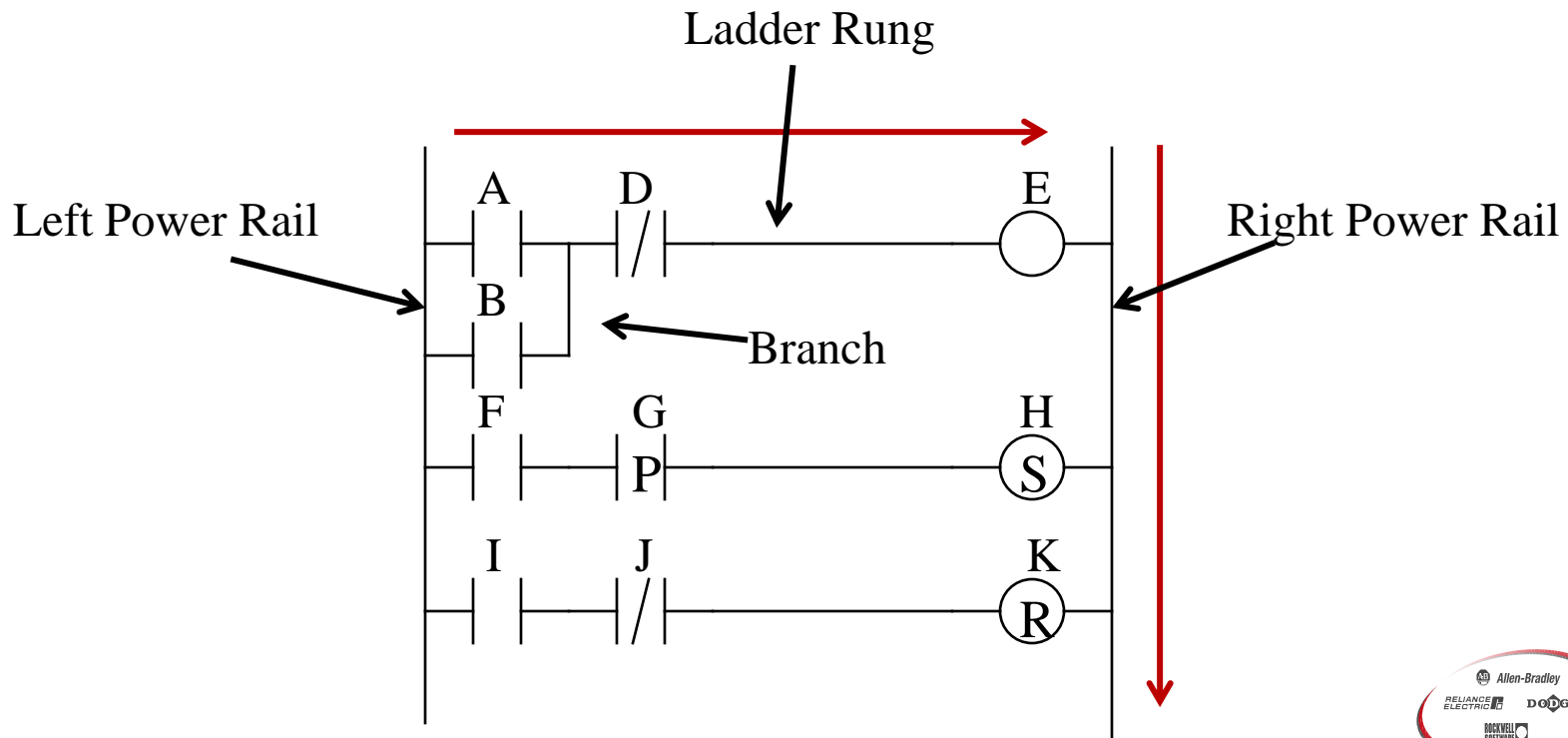- Rungs of Ladder diagram are solved from Left to right and top to bottom
- Branches within rungs are solved top left to bottom right



Non Retentive Coils

- The referenced bit is reset when processor power is cycled
 - Coil -()-
 - Sets a bit when the rung is true(1) and resets the bit when the rung is false (0)
 - PLC5 calls this an OTE Output Enable
 - Negative coil -(/)-
 - Sets a bit when the rung is false(0) and resets the bit when the rung is True(1)
 - Not commonly supported because of potential for confusion
 - Set (Latch) coil -(S)-
 - Sets a bit (1) when the rung is true and does nothing when the rung is false
 - Reset (Unlatch) Coil -(R)-
 - Resets a bit (0) when the rung is true and does nothing when the rung is false

Contacts

- Normally Open Contact -| |-
 - Enables the rung to the right of the instruction if the rung to the left is enabled and underlining bit is set (1)
- Normally Closed Contact -|/|-
 - Enables the rung to the right of the instruction if the rung to the left is enabled and underlining bit is reset (0)
- Positive transition contact -|P|-
 - Enables the right side of the rung for one scan when the rung on left side of the instruction is true
 - Allen Bradley PLC5 uses -[ONS]-
- Negative transition contact -|N|-
 - Enables the right side of the rung for one scan when the rung on left side of the instruction is false

Retentive Vs Non-retentive Operation

- Definitions
 - Retentive values or instructions maintain their last state during a power cycle
 - Non-retentive values or instructions are reset to some default state (usually 0) after a power cycle
- IEC1131 permits values to be defined as retentive
 - A contradiction to this is ladder diagram where 3 instructions are classified as retentive
 - In most PLCs only timer and coil instructions operate as non-retentive

Retentive Coils

- The referenced bit is unchanged when processor power is cycled
 - Retentive coil -(M)-
 - Sets a bit when the rung is true(1) and resets the bit when the rung is false (0)
 - Set Retentive (Latch) coil -(SM)-
 - Sets a bit (1) when the rung is true and does nothing when the rung is false
 - PLC5 uses OTL Output Latch
 - Reset Retentive (Unlatch) Coil -(RM)-
 - Resets a bit (0) when the rung is true and does nothing when the rung is false
 - PLC5 uses OUT Output Unlatch


Transition Sensing Coils

- Positive transition-sensing coil -(P)-
 - Sets the bit (1) when rung to the left of the instruction transitions from off(0) to on(1)
 - The bit is left in this state
 - PLC5 use OSR (One Shot Rising)
- Negative transition-sensing coil -(N)-
 - Resets the bit (0) when rung to the left of the instruction transitions from on(1) to off(0)
 - The bit is left in this state
 - PLC5 uses OSF (One Shot Falling)





IEC Comparison Instructions in Ladder

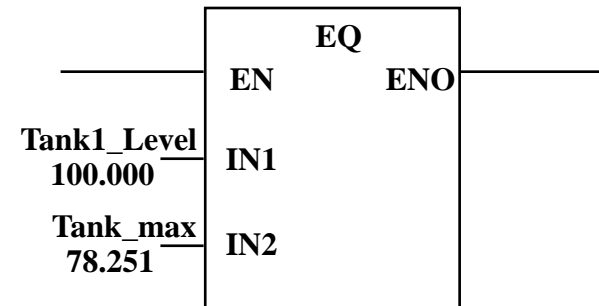- If the rung input (EN) is enabled, the instruction performs the operation and sets the rung output (ENO) based on the comparison
 - Example: when EN is true, EQ (=) function compares In1 and to In2 and sets ENO
- Comprehensive instruction set
 - EQ(=), GT (>), GE (>=), LT (<), LE (<=), NE (<>)






Timers in Ladder Diagram

- There three timer instructions in IEC1131
 - TP - Pulse timer
 - TON - Timer On Delay
 - TOF - Timer Off Delay
- Time values
 - Time base is 1msec (1/1000 of a sec)
 - Values entered using duration literal format
- Two possible visualizations Depending on use of EN/ENO
 - 1st method requires extra programming if timer done status needs to be referenced on other rungs
 - 2nd method sets a bit with Q which can be referenced by other logic, ENO=EN

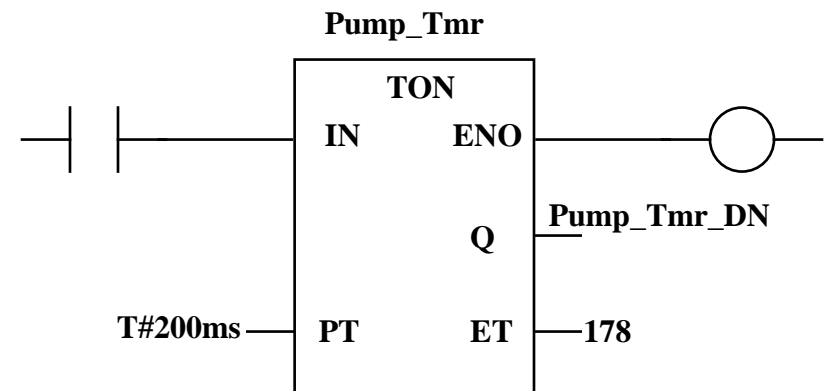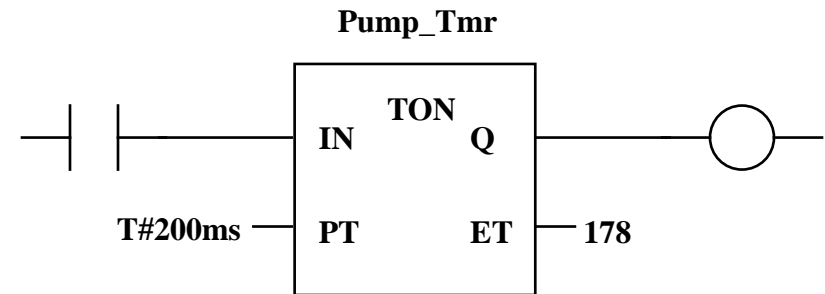



Timer Operation

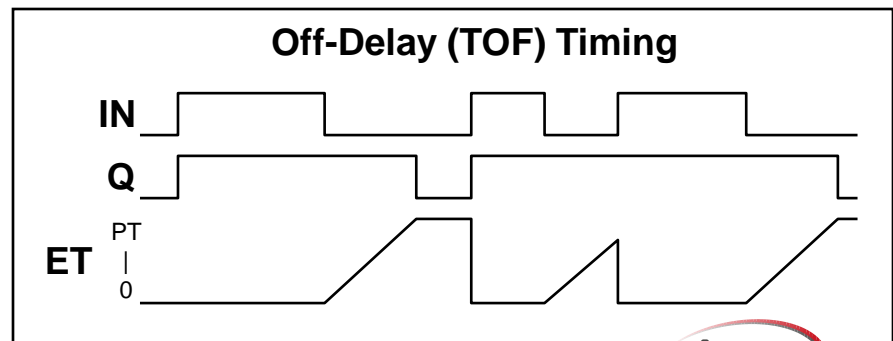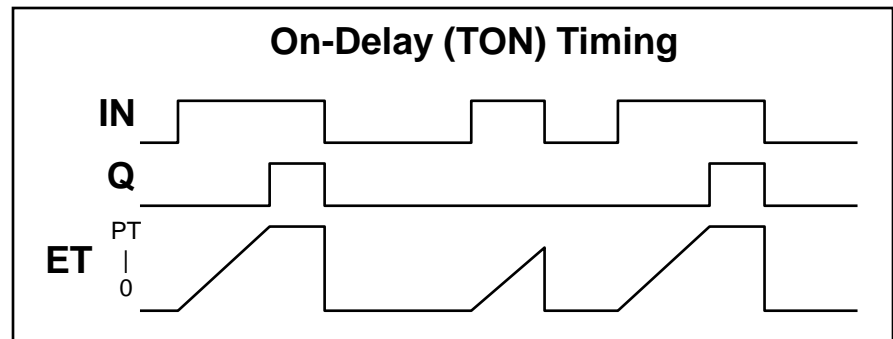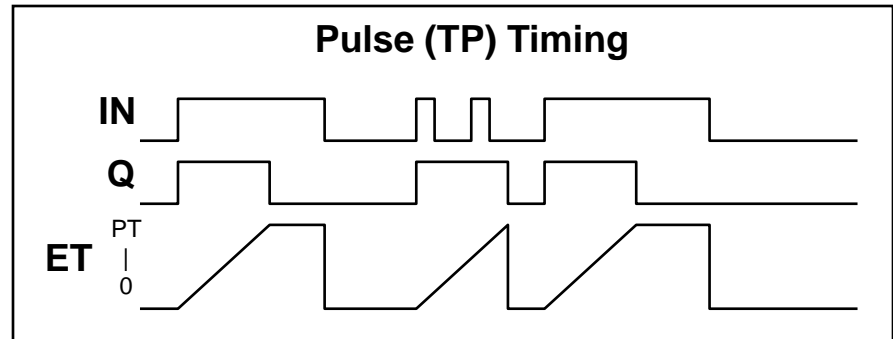- IN = Rung input condition
- Q = Comparison output results
 - Varies with timer types
- PT = Preset Time
- ET = Elapse Time






Counters in Ladder Diagram

- There three counter instructions in IEC1131
 - CTU - Count Up Counter
 - CTD - Count Down Counter
 - CTUD - Count Up/Down Counter
- All three count rung transitions
- Two possible visualizations
Depending on use of EN/ENO
 - 1st method requires extra programming if timer done status needs to be referenced on other rungs
 - 2nd method sets a bit with Q which can be referenced by other logic, ENO=EN

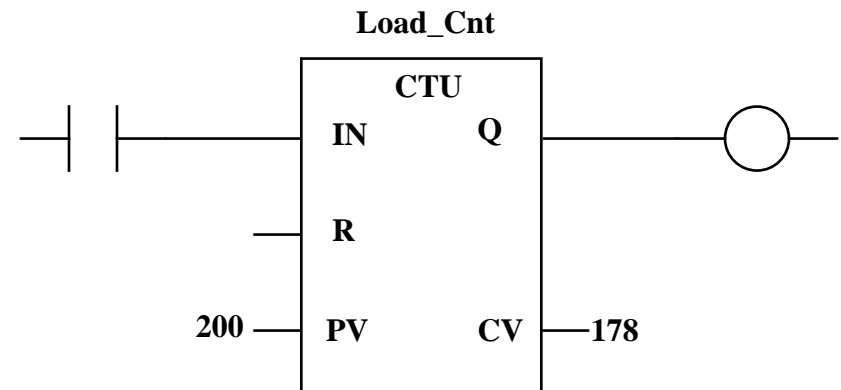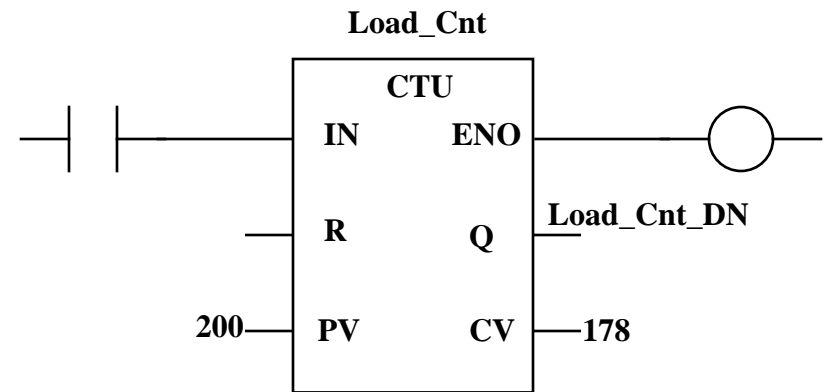

Counter Operation

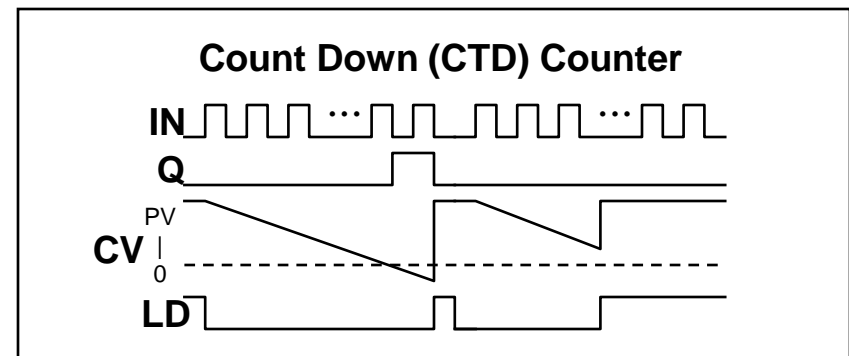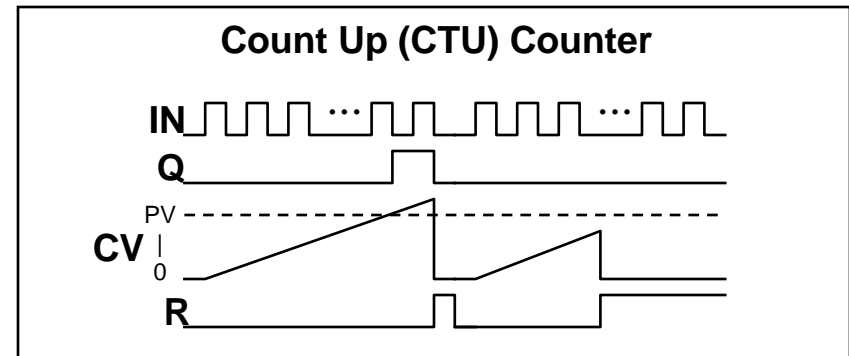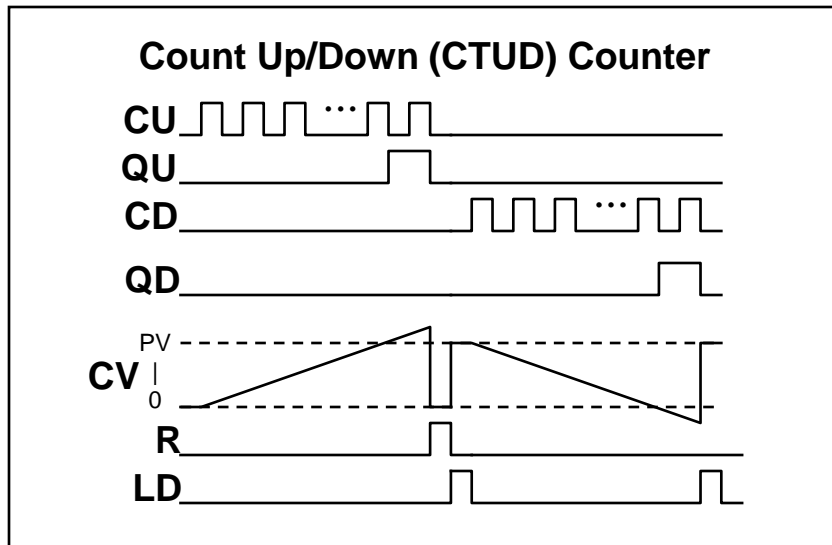
- Parameters
 - CU/CD = Count up/Down
 - Q/QU/QD = Comparison Output
 - R = Reset to Zero
 - LD = Load CV with PV
 - PV = Preset Value
 - CV = Count Value



Execution Control Elements


- Jump / Label Instructions

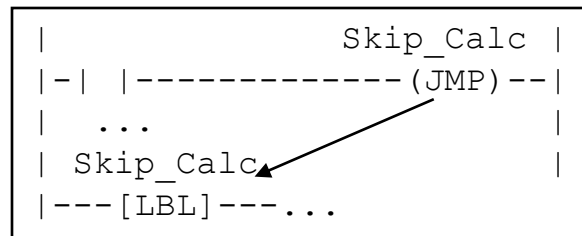- Jump to a label skips a block of code without it being scanned
- LBL - Named target for a jump operation
- JMP - Performs a jump when the rung conditions are true





- CALL / RETURN Instructions

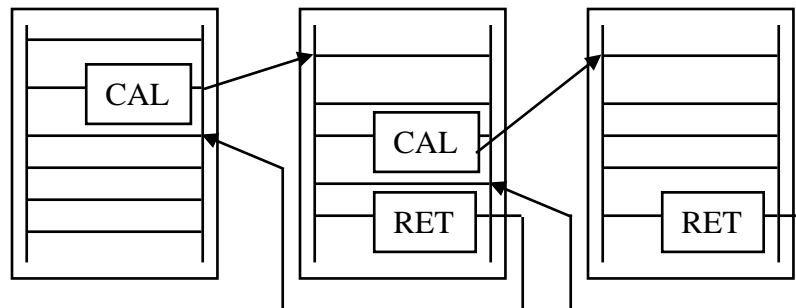- Used to encapsulate logic and call it as a subroutine
- Causes execution to change between functions or subroutines
- CAL - Passes control to another named function
 - PLC5 uses JSR
- RET - Exits a function and returns control back to the calling routine



Different Instruction Presentations

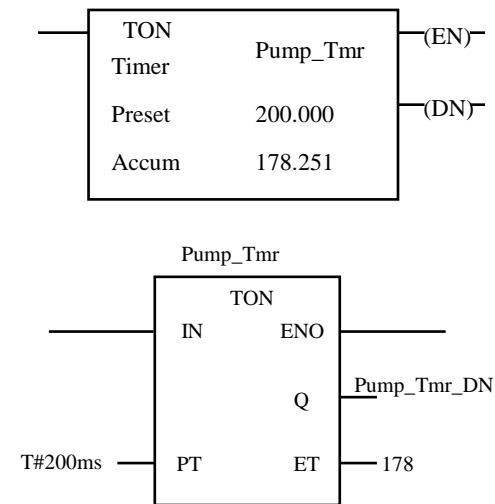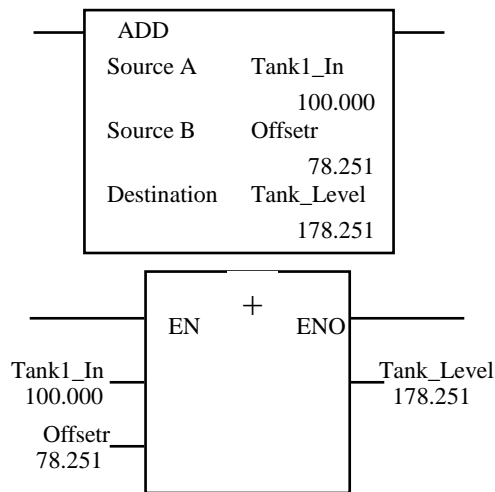- The look and feel of IEC 1131-3 is somewhat different from the 1Million+ PLC's that Allen Bradley has running in factories throughout the world




- IEC places the input parameters on the outside of the instruction block vs the PLC5 where they are presented inside of the block

Extending the IEC1131-3 Instruction Set

- IEC1131-3 Provides a very basic set of instructions to do simple operations (81 Ladder Diagram Instructions)
 - Data Type Conversion - Trunc, Int_to_Sint, Dint_to_Real, Bcd_To_Int ...
 - Boolean Operations - Bit Test, Bit Set, One Shot, Semaphores ...
 - Timers / Counters - Ton, Tp, Ctu, Ctd, Ctud
 - Simple Math - Add, Sub, Mul, Div, Mod, Move, Expt
 - Misc. Math - Abs, Sqrt, Ln, Log, Exp, Sin, Cos, Tan, Asin, Acos, Atan
 - Bit Shift - Shl, Shr, Ror, Rol
 - Logic - And, Or, Xor, Not
 - Selection - Sel, Max, Min, Limit, Mux
 - Compare - GT, GE, EQ, LE, LT, NE
 - String - Len, Left, Right, Mid, Concat, Insert, Delete, Replace, Find
 - Control - JMP, LBL, JSR, RET
- All complex operations are left to the user or vendor to define
 - File Operations, PID, Diagnostic, For/Nxt Loop, Search, Sort are not in IEC1131-3
 - Extensions to the instruction set are permitted so that vendors can add instructions that their customers need
 - All vendors have defined their own set of extensions
 - Rockwell Automation controllers have significantly more capability with over 130 Ladder Instructions




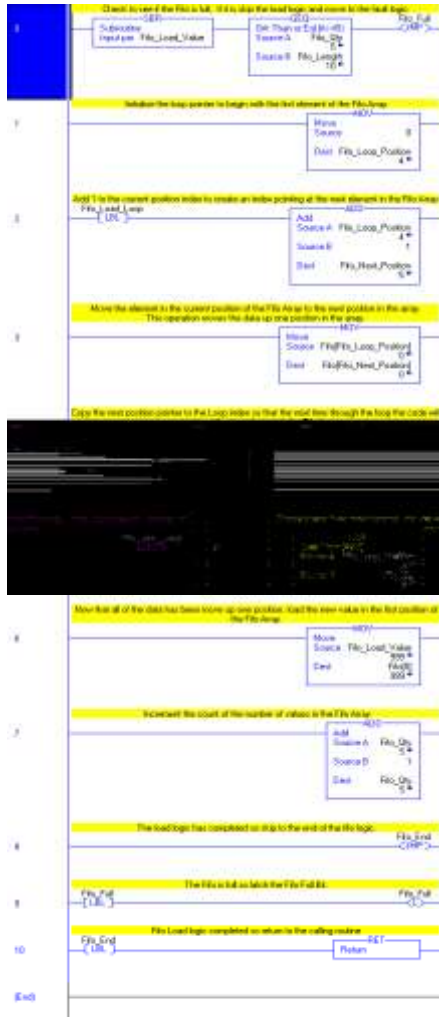Extensions to IEC provide code optimization and ease of use



=

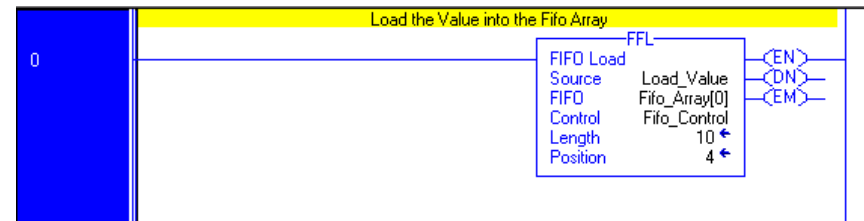Rockwell Automation FIFO Load Instruction



11 Rungs of Logic
17 Instructions
Hours to code and debug

1 Rung of Logic
1 Instruction
Minutes to code and debug

Rockwell Automation

Instruction Extension to IEC1131-3

- FIFO & LIFO - FFL, FFU, LFL, LFU
- File math and search - FAL, FSC
- Table operations - SRT, STD, AVE
- Sequencers - SQI, SQL, SQO, SDS
- Diagnostics - DDT, DFA, FBC
- Compare - CMP, MEQ
- Compute - CPT, NEG
- Data moves - MVM, COP, BTD
- Program Control - AFI, NOP, MCR, TND
- Interrupt Services - UID, UIE
- Retentive Timer - RTO
- Ladder Loop Instruction - FOR, NXT
- Process - PID
- Motion - 30+ instructions to perform closed loop servo control